

ELEMENTARY ELECTRICAL
ENGINEERING

ALBERT E. CLAYTON
AND
HERBERT J. SHEELEY

ELEMENTARY ELECTRICAL ENGINEERING

BY

ALBERT E. CLAYTON

D.Sc. (ENGINEERING) LOND.

ASSOCIATE OF KING'S COLLEGE; M.I.E.E.

FORMERLY SENIOR LECTURER IN ELECTRICAL ENGINEERING
IN THE VICTORIA UNIVERSITY, AT THE COLLEGE
OF TECHNOLOGY, MANCHESTER

AND

HERBERT J. SHELLEY

C.B., O.B.E., B.Sc. MANCHESTER, A.M.I.E.E.

FORMERLY ASSISTANT LECTURER IN ELECTRICAL ENGINEERING
IN THE VICTORIA UNIVERSITY, AT THE COLLEGE
OF TECHNOLOGY, MANCHESTER

WITH DIAGRAMS



LONGMANS, GREEN AND CO
LONDON · NEW YORK · TORONTO

CONTENTS

CHAPTER I

	PAGE
The Electric Circuit—Series and Parallel Grouping—Specific Resistance—Temperature Coefficient—Power and Energy—Units	1

CHAPTER II

Magnetic Effects of Current—Magnetic Circuit—Magnetic Properties of Materials	20
---	----

CHAPTER III

Electromagnetic Induction—Elementary Theory of the Dynamo—E.M.F. Equation—Magnetic Circuit of the Direct-current Machine	39
--	----

CHAPTER IV

Direct-current Armature Windings	62
--	----

CHAPTER V

The Direct-current Generator—Separate and Self-excitation—Shunt, Series, and Compound Windings—Armature Reaction—Load Characteristics	82
---	----

CHAPTER VI

Inductance—E.M.F. of Self-induction—Inductance Effects in Direct-current Circuits—Commutation in Direct-current Machines	107
--	-----

CHAPTER VII

Direct-current Motors	121
---------------------------------	-----

CHAPTER VIII

Alternating Currents—Frequency—Virtual Value—Phase Dis- placement—Vector Diagrams	PAGE 140
--	-------------

CHAPTER IX

Alternating Currents (<i>continued</i>)—Inductance—Reactance—Im- pedance—Circuits possessing Resistance and Inductance	174
---	-----

CHAPTER X

Power in Alternating-current Circuits—Mean Power—Apparent Power—Power Factor	191
---	-----

CHAPTER XI

Capacitance—The General Series Circuit—Voltage Resonance —Simple Parallel Circuits	200
---	-----

CHAPTER XII

Polyphase Circuits—Star and Mesh Connections—Power in Three-phase Circuits—4-wire System	229
---	-----

CHAPTER XIII

Choking Coils—The Single-phase Transformer	244
--	-----

CHAPTER XIV

Measuring Instruments—Principles—Ammeters, Voltmeters, Wattmeters, and Ohmmeters—Integrating Meters— Measurements, the Potentiometer—Wheatstone's Bridge— Substitution Methods	260
---	-----

CHAPTER XV

Chemical Effects—Electrolysis, Primary Cells—The Lead Storage Cell—The Alkaline Cell—Charging of Storage Cells	297
--	-----

